 


Máquina Multinivel

y Lógica Digital

Fundamentos de
Arquitectura de Computadoras



Recursos de una computadora



CPU - Procesador

Encargado de ejecutar las instrucciones y procesar los datos.



Memoria Principal - RAM

Almacenamiento de acceso rápido y temporal para los programas en ejecución.




Dispositivos de Entrada/Salida

Periféricos de interacción y almacenamiento secundario permanente para preservar la información.





Información (Software)

El conjunto de programas y datos.

 

Placa Madre (Motherboard)

  



Máquina multinivel

Máquina multinivel

NIVEL 5

Nivel de lenguaje orientado al problema

Traducción (Compilador)

NIVEL 4

Nivel de lenguaje ensamblador

Traducción (Ensamblador)

NIVEL 3

Nivel de máquina del sistema operativo

Interpretación parcial (S.O.)

NIVEL 2

Nivel de máquina convencional

Interpretación o Ejecución Directa


NIVEL 1

Nivel de microarquitectura

Ejecución directa por el Hardware

NIVEL 0

Nivel de lógica digital

 

Programa en diferentes niveles

LENGUAJE DE ALTO NIVEL

```
int m[256];  
int main() {  
    int* i = &m[0];  
    int c = 3;  
    *(i+1) = 1;  
    do {  
        *(i+1) *= c;  
        c--;  
    } while (c != 0);  
    printf("%d\n", *(i+1));  
}
```

SE COMPILA

COMPILADOR

LENGUAJE MÁQUINA



	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
00000000	50	10	D0	B0	00	01	00	04	D0	90	00	03	CC	74	CC	00
00000010	04	D0	91	FF	FF	CC	85	00	0D	90	00	01	A4	90	04	01
00000020	CC	91	00	04	D0	80	00	02	0F	+						

SE INTERPRETA

Programa en diferentes niveles

LENGUAJE DE ALTO NIVEL

```
int m[256];
int main() {
    int* i = &m[0];
    int c = 3;
    *(i+1) = 1;
    do {
        *(i+1) *= c;
        c--;
    } while (c != 0);
    printf("%d\n", *(i+1));
}
```

SE COMPILA

LENGUAJE ASSEMBLER

```
mov     edx, ds
mov     [edx+4], 1
mov     cx, 3
otro:   mul     [edx+4], cx
        add     cx, -1
        jnz     otro
fin:    mov     al, 1
        mov     cx, 0x0401
        add     edx, 4
        sys     0x2
        stop
```

SE TRADUCE

LENGUAJE MÁQUINA



	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
00000000	50	10	D0	B0	00	01	00	04	D0	90	00	03	CC	74	CC	00
00000010	04	D0	91	FF	FF	CC	85	00	0D	90	00	01	A4	90	04	01
00000020	CC	91	00	04	D0	80	00	02	0F	+						

SE INTERPRETA

Programa en diferentes niveles

LENGUAJE DE ALTO NIVEL

```
int m[256];
int main() {
    int* i = &m[0];
    int c = 3;
    *(i+1) = 1;
    do {
        *(i+1) *= c;
        c--;
    } while (c != 0);
    printf("%d\n", *(i+1));
}
```

LENGUAJE ASSEMBLER

```
mov     edx, ds
mov     [edx+4], 1
mov     cx, 3
otro:   mul     [edx+4], cx
        add     cx, -1
        jnz     otro
fin:    mov     al, 1
        mov     cx, 0x0401
        add     edx, 4
        sys     0x2
        stop
```

LENGUAJE MÁQUINA



	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
00000000	50	10	D0	B0	00	01	00	04	D0	90	00	03	CC	74	CC	00
00000010	04	D0	91	FF	FF	CC	85	00	0D	90	00	01	A4	90	04	01
00000020	CC	91	00	04	D0	80	00	02	0F	+						

Programa en diferentes niveles

LENGUAJE DE ALTO NIVEL

```
int m[256];
int main() {
    int* i = &m[0];
    int c = 3;
    *(i+1) = 1;
    do {
        *(i+1) *= c;
        c--;
    } while (c != 0);
    printf("%d\n", *(i+1));
}
```

LENGUAJE ASSEMBLER

```
mov     edx, ds
mov     [edx+4], 1
mov     cx, 3
otro:   mul     [edx+4], cx
        add     cx, -1
        jnz     otro
fin:    mov     al, 1
        mov     cx, 0x0401
        add     edx, 4
        sys     0x2
        stop
```

LENGUAJE MÁQUINA



	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
00000000	50	10	D0	B0	00	01	00	04	D0	90	00	03	CC	74	CC	00
00000010	04	D0	91	FF	FF	CC	85	00	0D	90	00	01	A4	90	04	01
00000020	CC	91	00	04	D0	80	00	02	0F	+						

Programa en diferentes niveles

LENGUAJE DE ALTO NIVEL

```
int m[256];
int main() {
    int* i = &m[0];
    int c = 3;
    *(i+1) = 1;
    do {
        *(i+1) *= c;
        c--;
    } while (c != 0);
    printf("%d\n", *(i+1));
}
```

LENGUAJE ASSEMBLER


```
mov     edx, ds
mov     [edx+4], 1
otro:   mov     cx, 3
        mul     [edx+4], cx
        add     cx, -1
        jnz     otro
fin:    mov     al, 1
        mov     cx, 0x0401
        add     edx, 4
        sys     0x2
        stop
```

LENGUAJE MÁQUINA



	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
00000000	50	10	D0	B0	00	01	00	04	D0	90	00	03	CC	74	CC	00
00000010	04	D0	91	FF	FF	CC	85	00	0D	90	00	01	A4	90	04	01
00000020	CC	91	00	04	D0	80	00	02	0F	+						

Memoria

 

Celda

Byte

Dirección

Direccionamiento

Figure 2-9. Three ways of organizing a 96-bit memory.

Memoria

 


Figure 2-9. Three ways of organizing a 96-bit memory.

Memoria


 


Figure 2-9

 

Lógica Digital

Compuertas lógicas

 


Figure 3-2. The symbols and functional behavior for the five basic gates.

Chip



 
 


Figure 3-10. An SSI chip containing four gates.


Multiplexor (1 bit)

 



Multiplexor (1 bit)

 

Multiplexor (1 bit)

 

Multiplexor (2 bits)

  

Decodificador (3 bits)

 
 


Figure 3-13. A 3-to-8 decoder circuit.

Sumador (1 bit)

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


 


Figure 3-17. (a) Truth table for 1-bit addition. (b) A circuit for a half adder.

Sumador (1 bit con carry in)

A	B	Carry in	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(a)

 

(b)

Figure 3-18. (a) Truth table for full adder. (b) Circuit for a full adder.

Unidad Aritmético Lógica (ALU)


 


Figure 3-20. Eight 1-bit ALU slices connected to make an 8-bit ALU. The enables and invert signals are not shown for simplicity.

Unidad Aritmético Lógica (ALU)

 


00 = $A + B$

01 = $A \& B$

10 = Copia A

11 = Complemento A

Shifter

 

00 = No Shift

01 = Shift Right 1 bit

10 = Shift Left 1 bit

11 = (sin uso)

Clock


 
 


Figure 3-21. (a) A clock. (b) The timing diagram for the clock. (c) Generation of an asymmetric clock.

Clock

 

Flip Flops

 


Figure 3-23. A clocked SR latch.

Flip Flops

 


Figure 3-23. A clocked SR latch.

Flip Flops

 


Figure 3-23. A clocked SR latch.

Flip Flops

 


Figure 3-23. A clocked SR latch.

Flip Flops

 


Figure 3-23. A clocked SR latch.

Flip Flops

 


Figure 3-23. A clocked SR latch.

Flip Flops

 


Figure 3-23. A clocked SR latch.

Flip Flops

 


Figure 3-23. A clocked SR latch.

Registro

Bit Number	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
	0	0	0	0	1	1	0	0	1	0	1	1	0	0	1	0

Fig 4-1. A 16-bit register can hold 16 bits of information

 


Fig 4-2 (a) Detail of an 8-bit register connected to an input bus and an output bus

Registro

Bit Number	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
	0	0	0	0	1	1	0	0	1	0	1	1	0	0	1	0

Fig 4-1. A 16-bit register can hold 16 bits of information


 


Fig 4-2 (b) Symbolic representation of a 16-bit register with one input bus and two output buses

Uniendo algunas piezas

 

Máquina multinivel

NIVEL 5

Nivel de lenguaje orientado al problema

Traducción (Compilador)

NIVEL 4

Nivel de lenguaje ensamblador

Traducción (Ensamblador)

NIVEL 3

Nivel de máquina del sistema operativo

Interpretación parcial (S.O.)

NIVEL 2

Nivel de máquina convencional

Interpretación o Ejecución Directa


NIVEL 1

Nivel de microarquitectura

Ejecución directa por el Hardware

NIVEL 0

Nivel de lógica digital

 

Máquina Multinivel

y Lógica Digital

Fundamentos de
Arquitectura de Computadoras

